
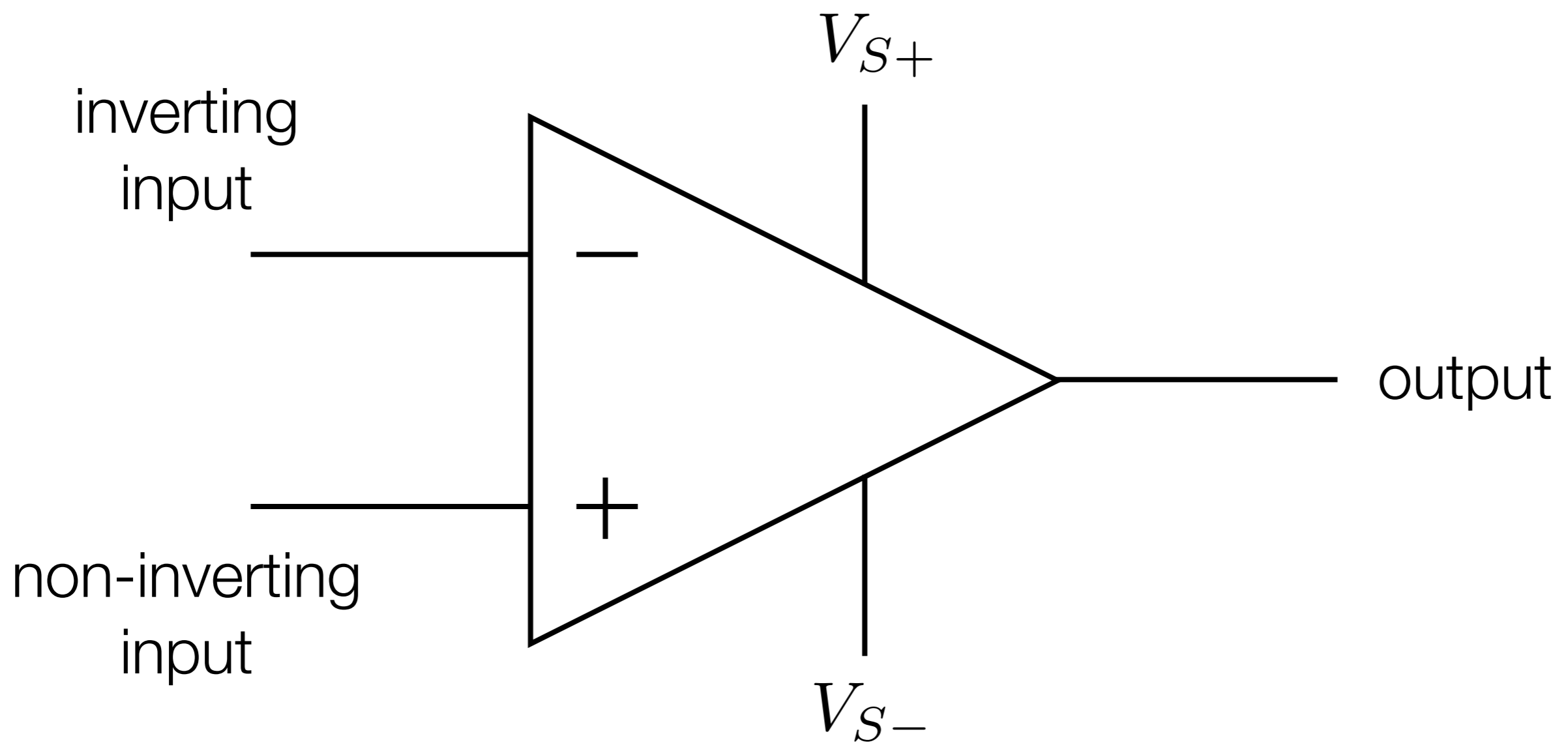


# Operational Amplifiers

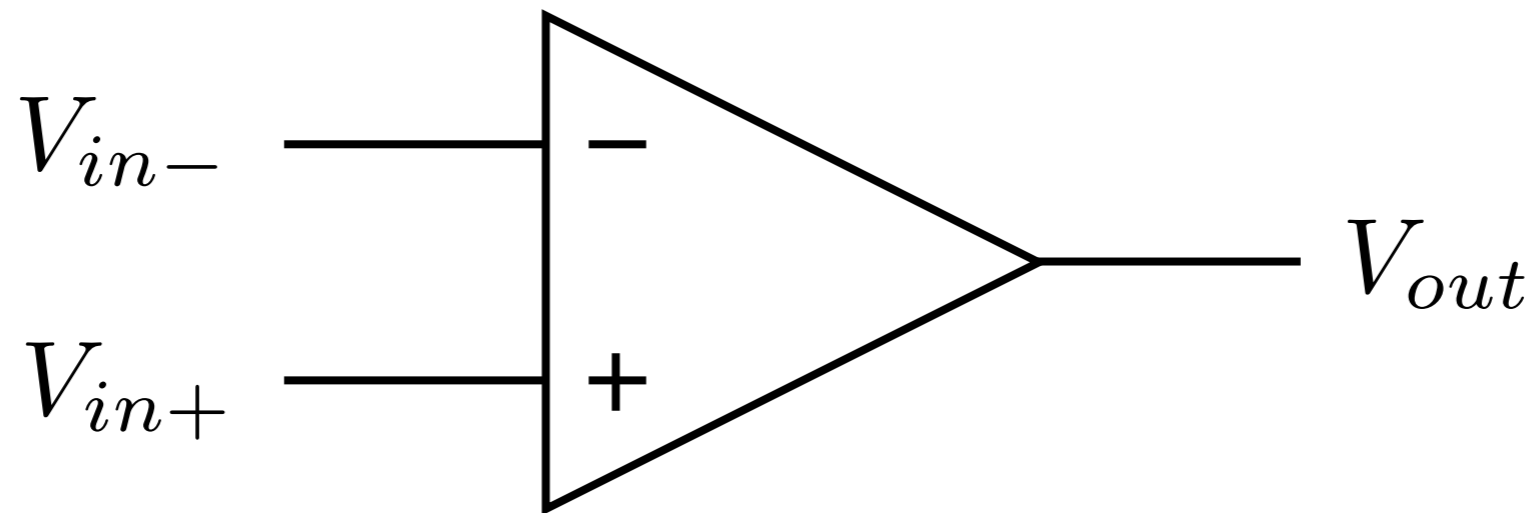




output = amplified difference between inputs




$$V_{out} = (V_{+} - V_{-})A$$

where the gain is typically extremely large


$$A \geq 10^5$$

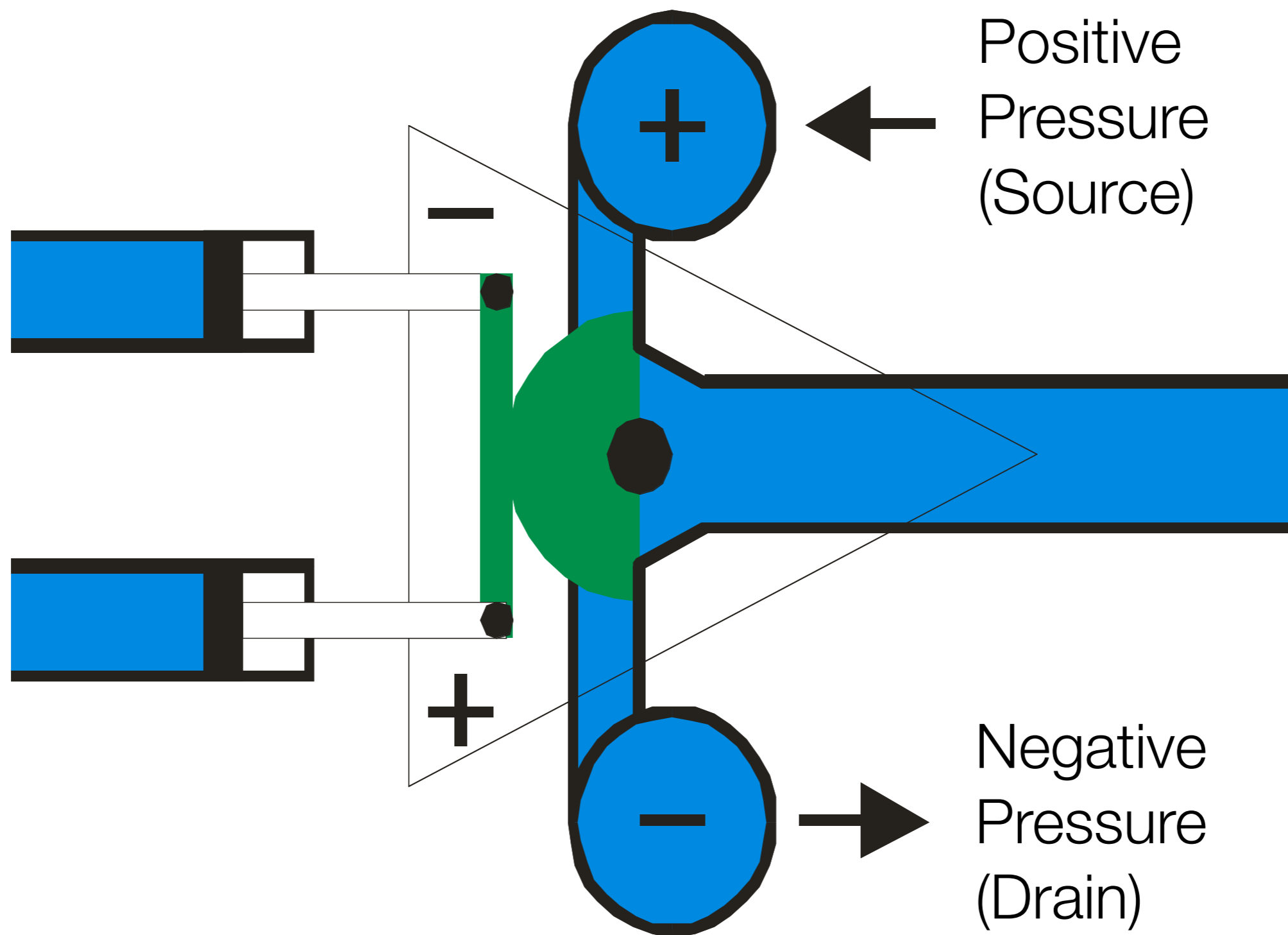

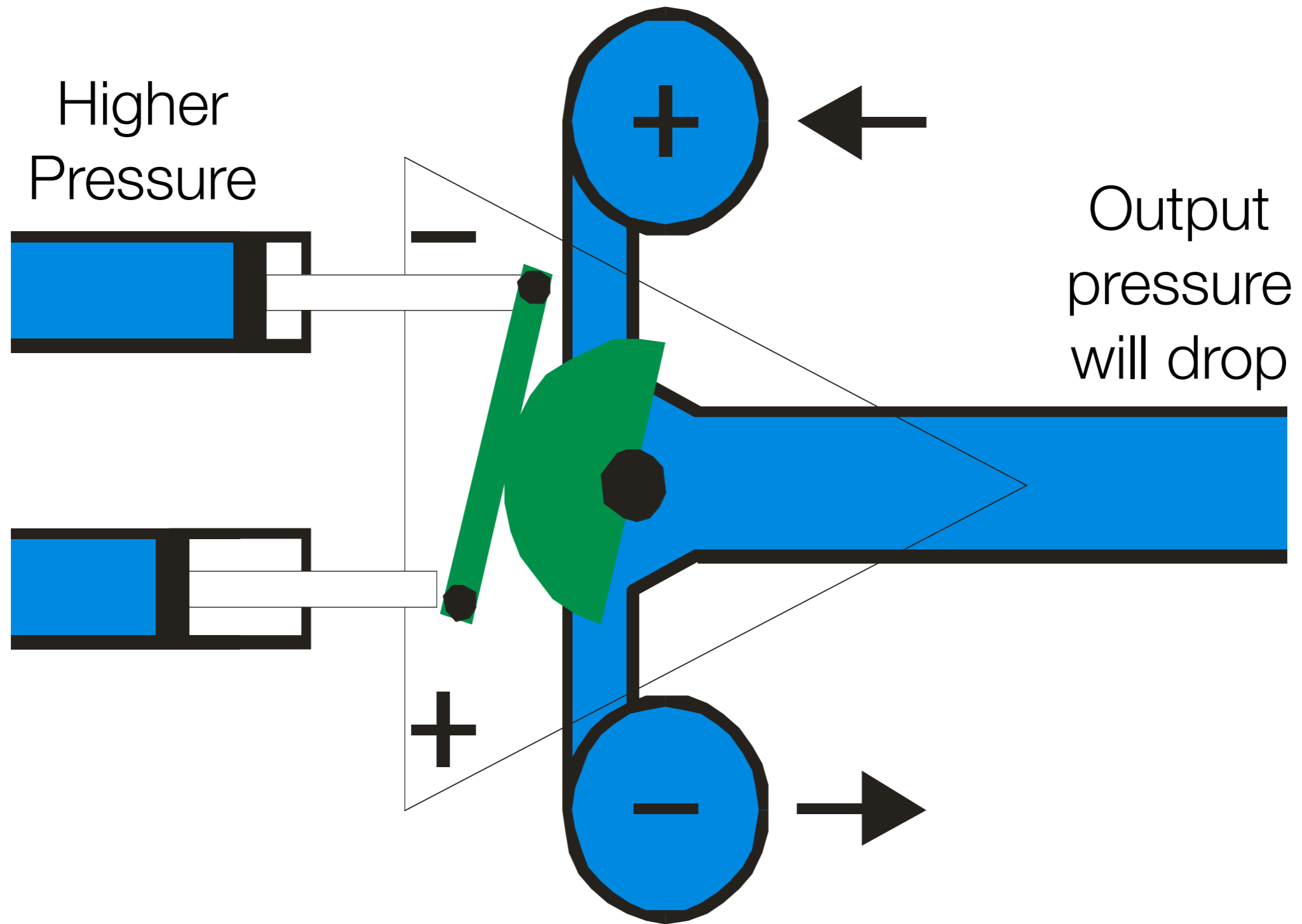

Higher Pressure

Output pressure will drop

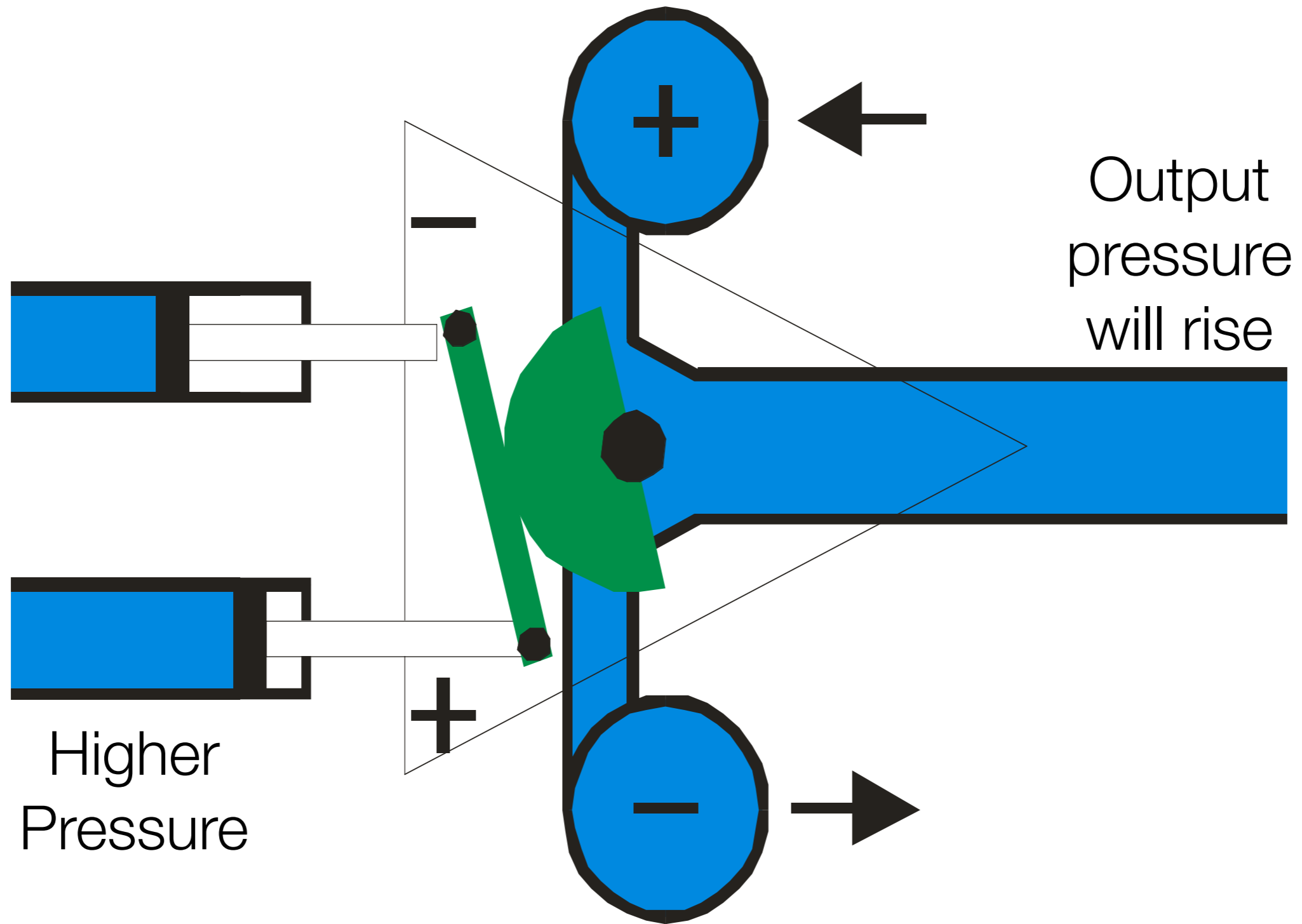


Higher  
Pressure

Output  
pressure  
will rise

input impedance is very high  $R_{in} \approx 4M\Omega$

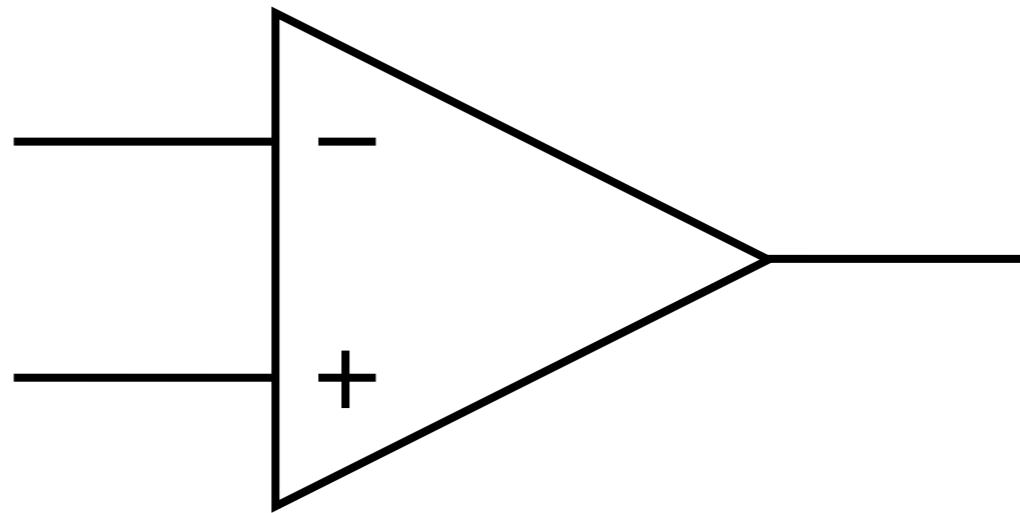output impedance is very low  $R_{out} \approx 100\Omega$



very high bandwidth

For most op-amp circuits, we can safely assume:

**infinite gain**


**infinite input impedance**

**zero output impedance**

**zero input offset voltage**




The first golden rule of op amps

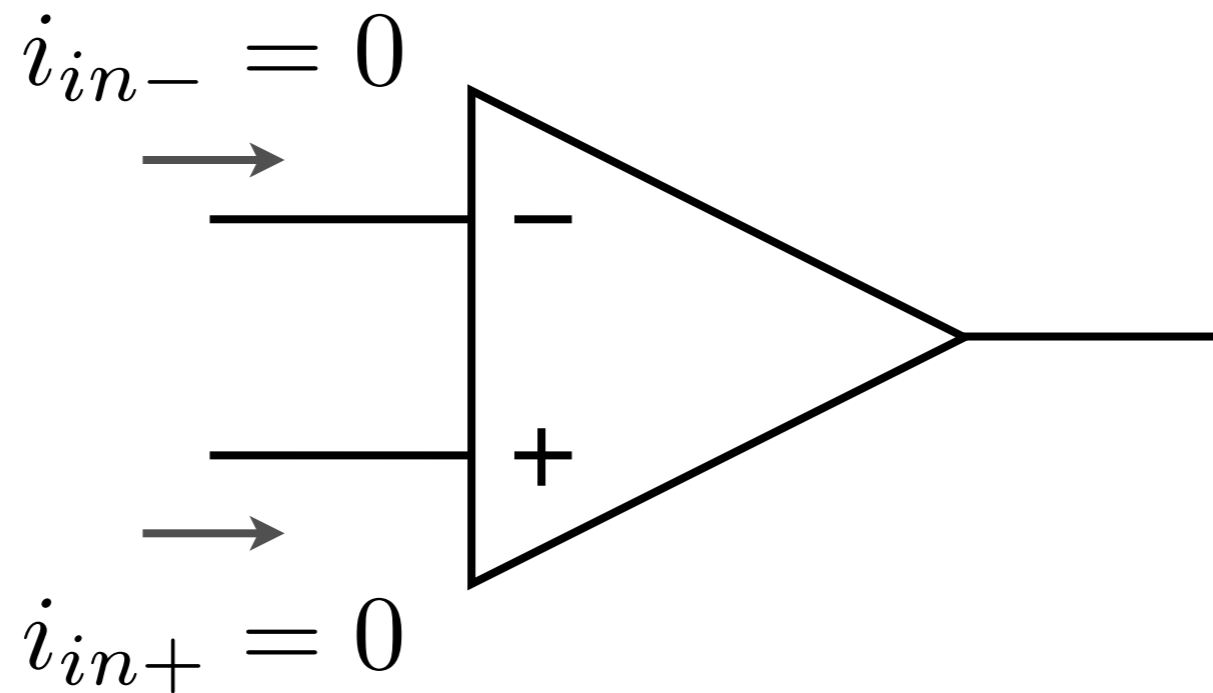


**THE INPUTS DRAW “NO” CURRENT**


The second golden rule of op amps

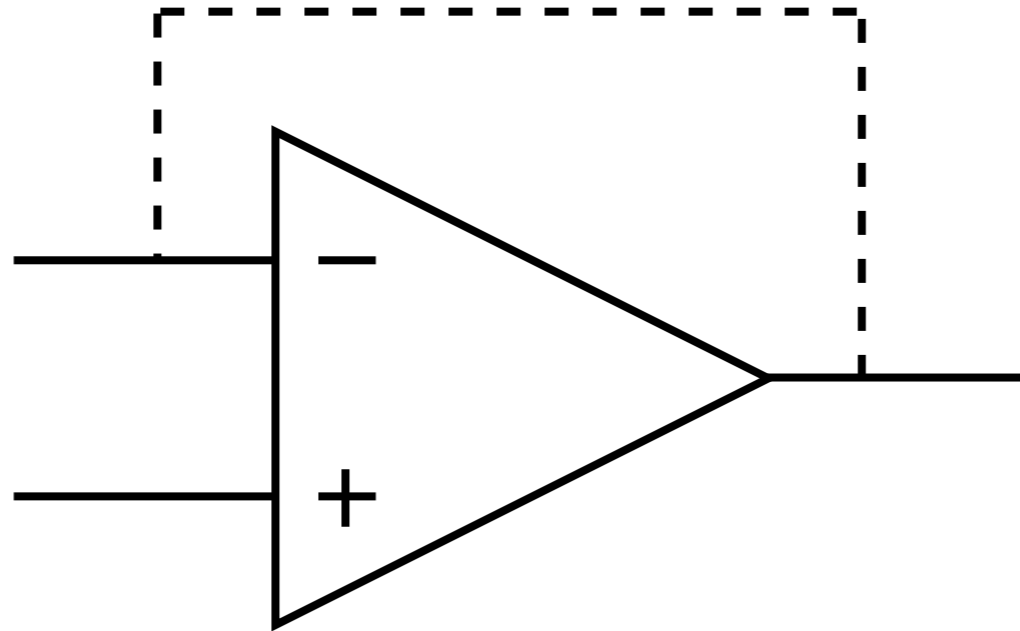

**IN NEGATIVE FEEDBACK,**

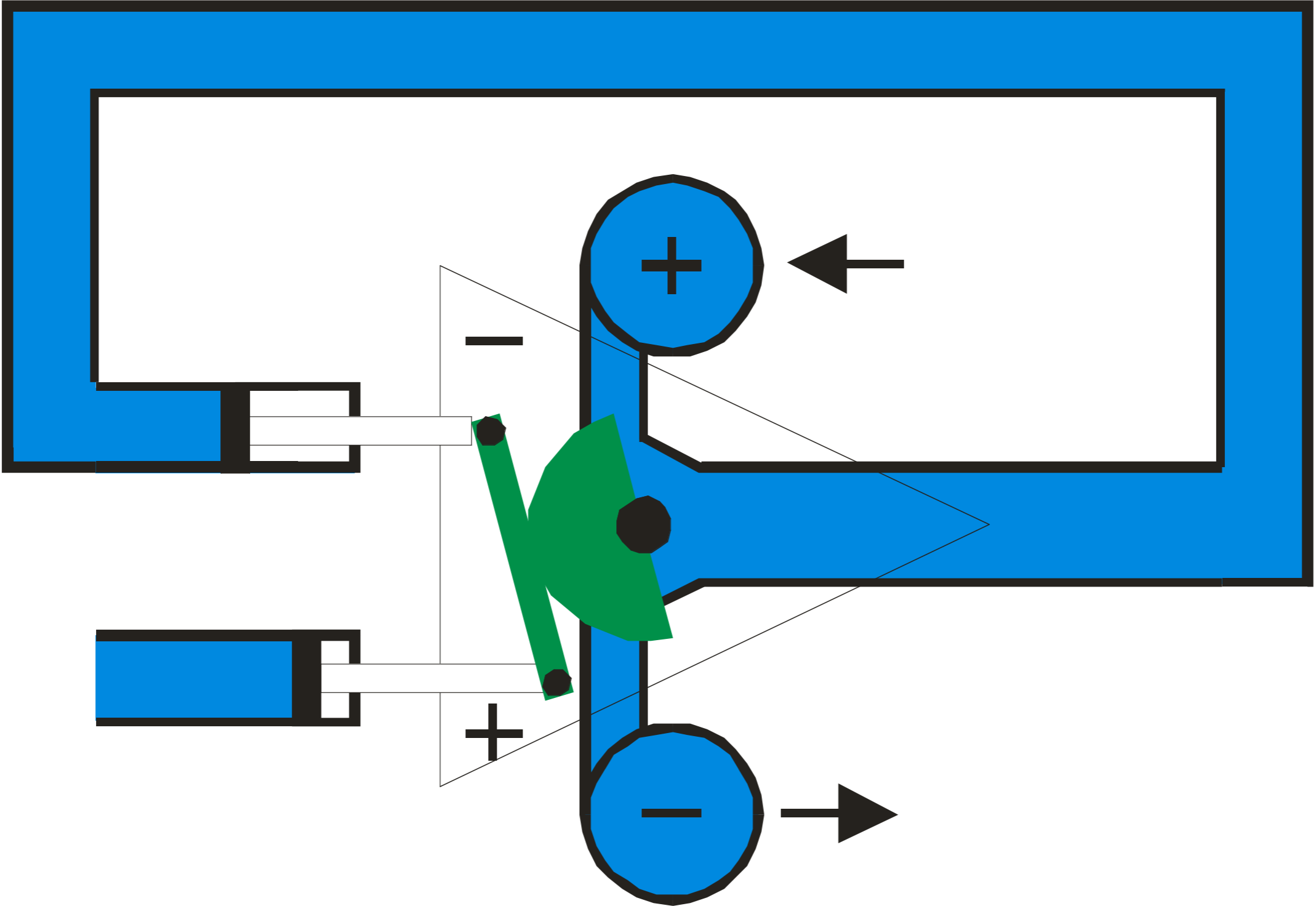
**THE INPUT VOLTAGES WILL BE “THE SAME”**



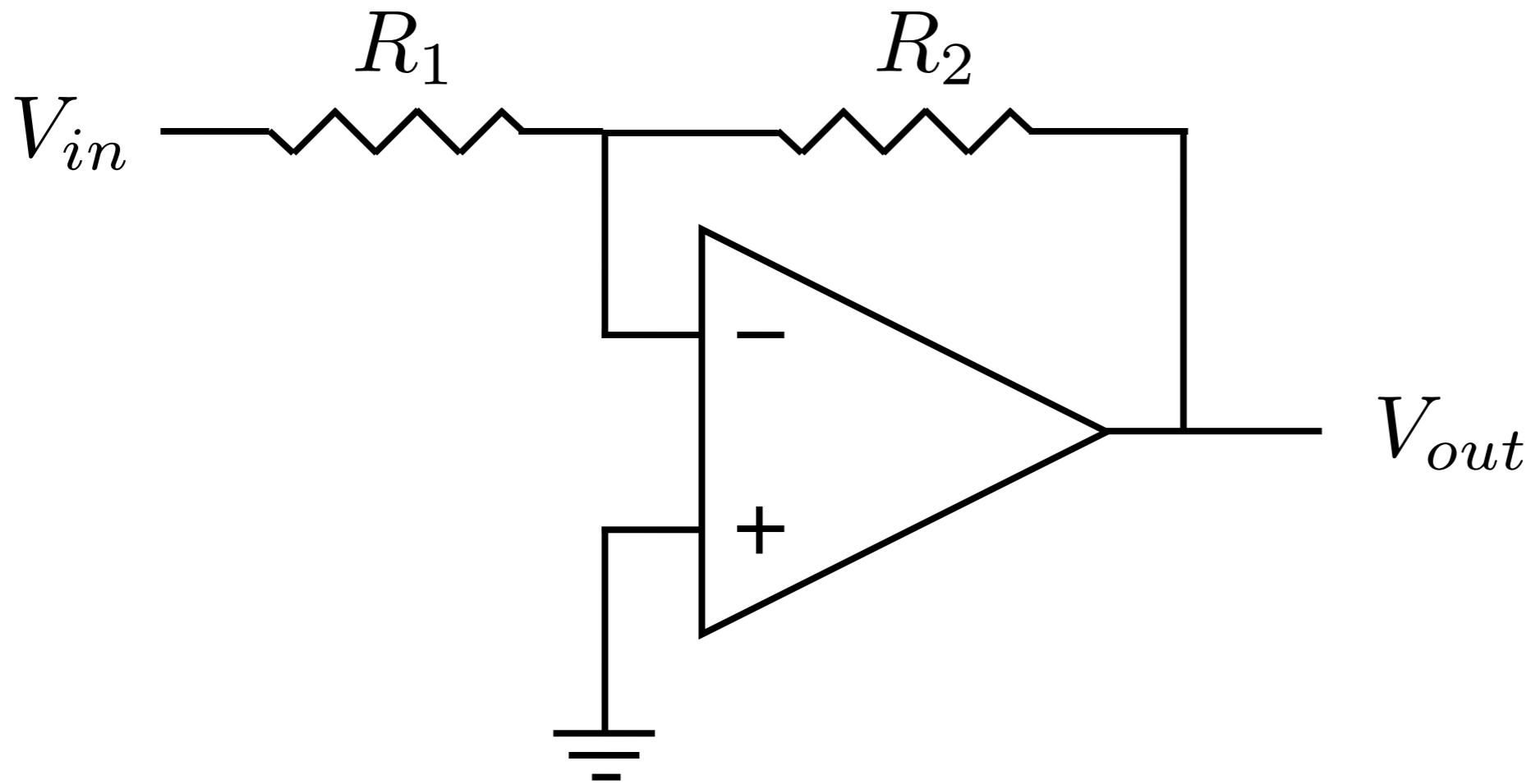


$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Standard "Inverting" Configuration

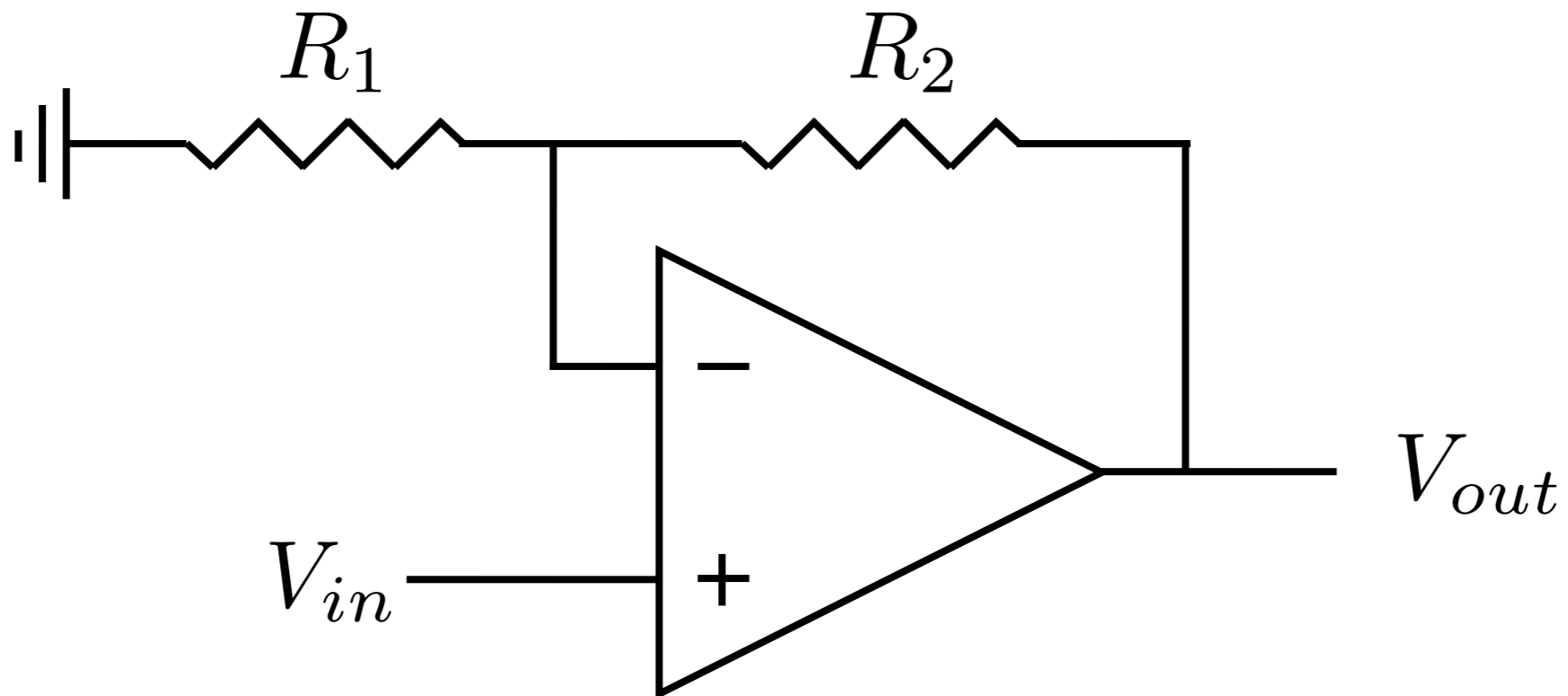

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

Standard “Non-Inverting” Configuration

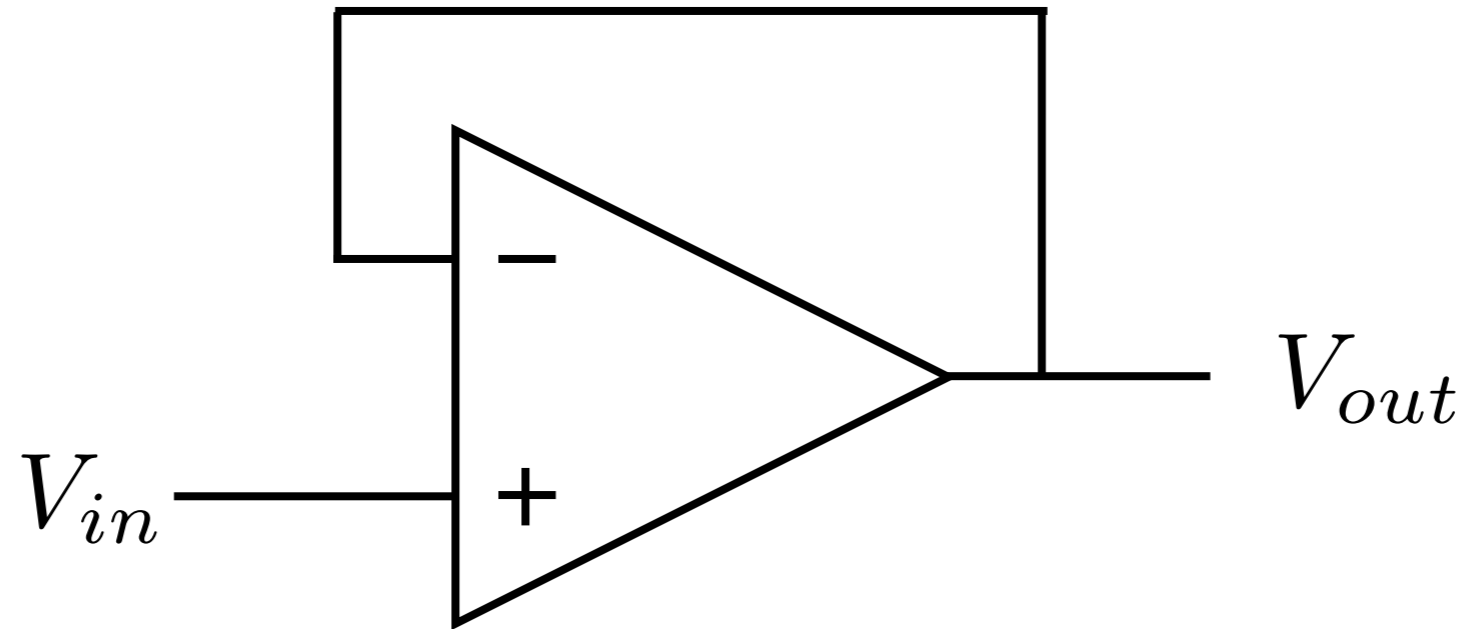


$$V_{out} = V_{in}$$

Standard "Buffer" Configuration

A challenge:

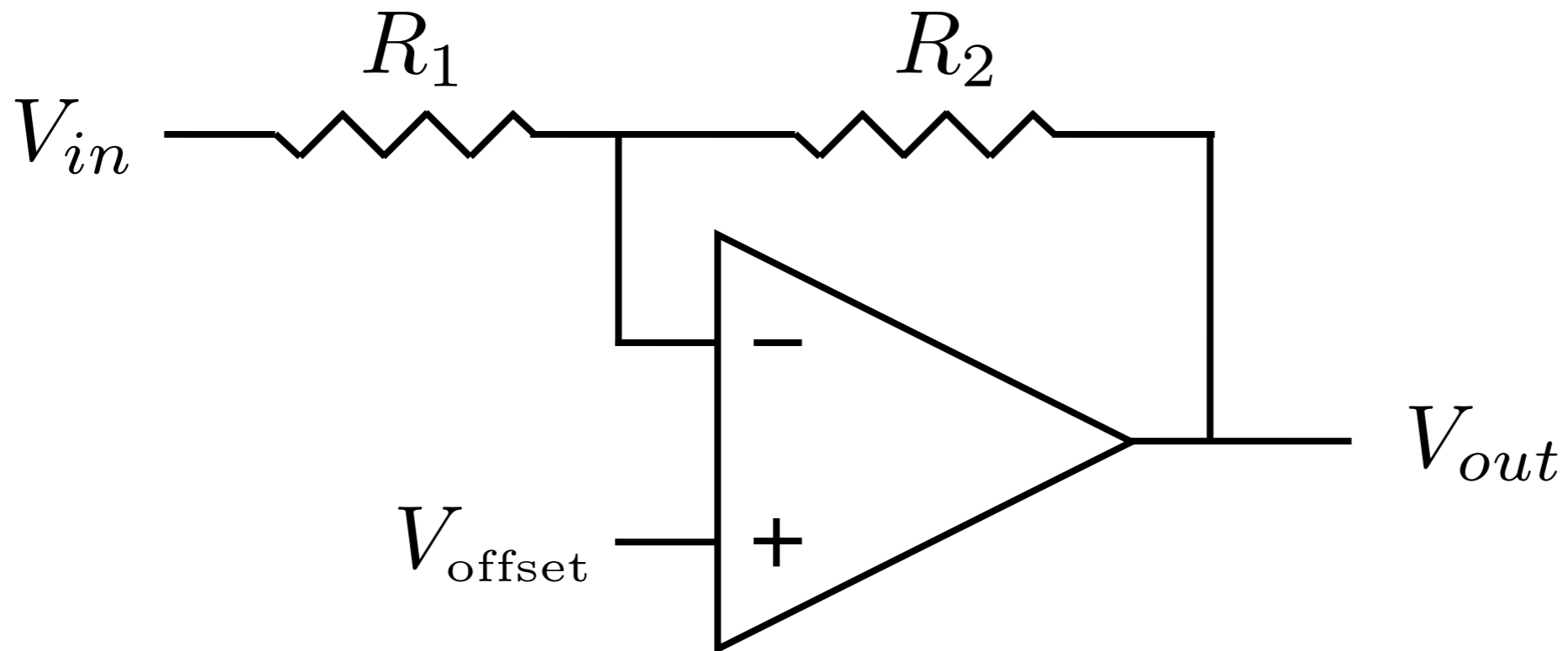We have a 200 mV (peak-to-peak) sinusoidal signal that we want to amplify to 1 V (peak-to-peak) while maintaining phase.



$$V_{out} = V_{offset} \left( 1 + \frac{R_2}{R_1} \right) - V_i \frac{R_2}{R_1}$$

Inverting with Offset




# Op Amp Design Methodology

determine whether you want inversion

choose the gain

determine offset

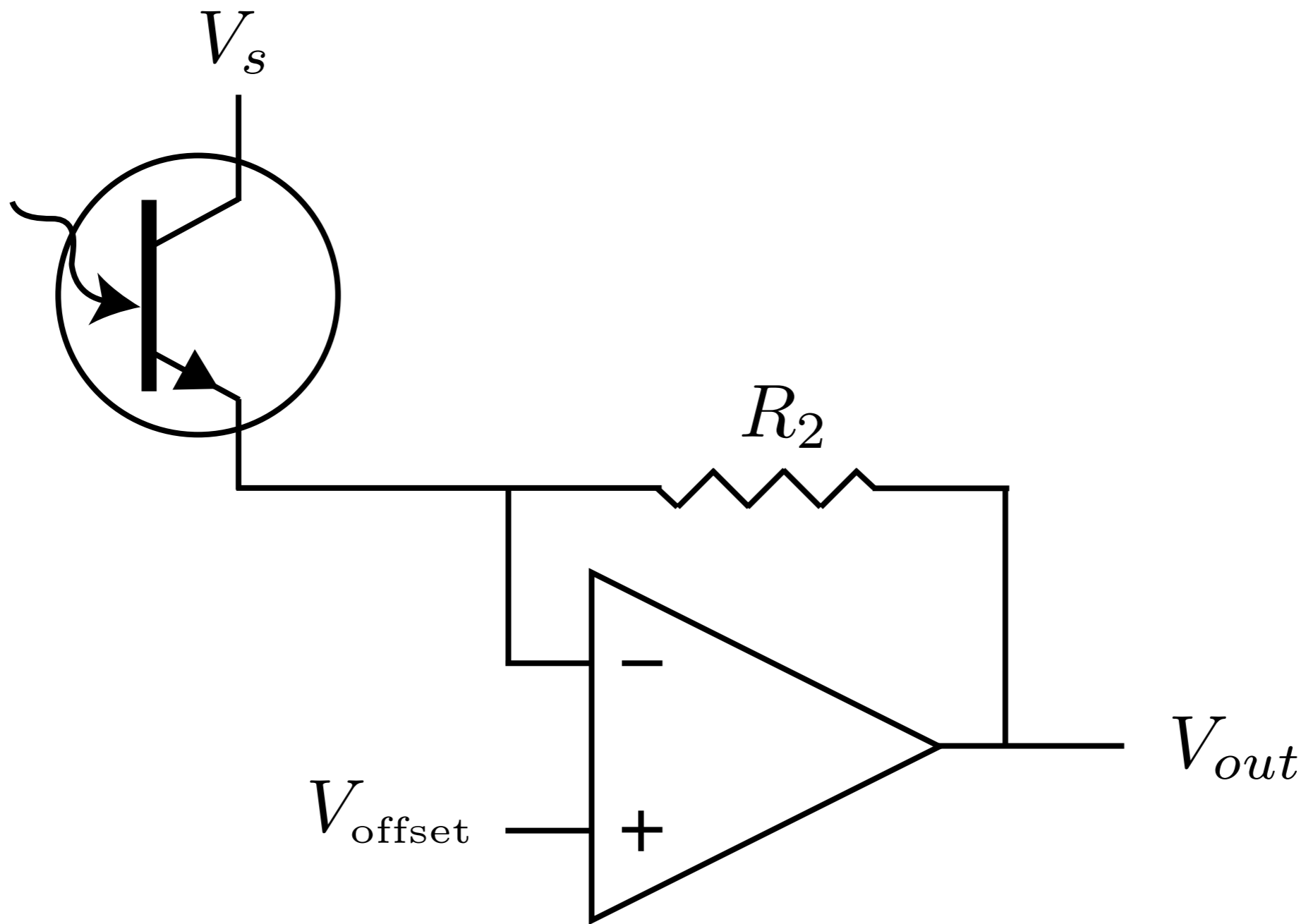

$$V_{\text{out}} = V_{\text{offset}} - R_2 i_{\text{photo}}$$

	qty	supply	CMMR	R-to-R	iO (mA)	cost
LM358	dual	3-32V $\pm 1.5-16V$	80 dB	N	8 / 20	\$0.24
TLV272	dual	2.7-16V $\pm 1.35-8V$	85 dB	Y	7 / 8	\$0.56
TLC2272	dual	$\pm 8V$	75 dB	Y	50 / 50	\$0.82
TCA0372	dual	0-40V $\pm 20V$	90 dB	~Y	1000	\$0.83
LM324	quad	3-32V $\pm 1.5-16V$	85 dB	N	20 / 40	\$0.27
LM6142	dual	0-35V	107 dB	Y	25 / 25	\$0.60
LM6144	quad	$\pm 17.5V$				\$1.07