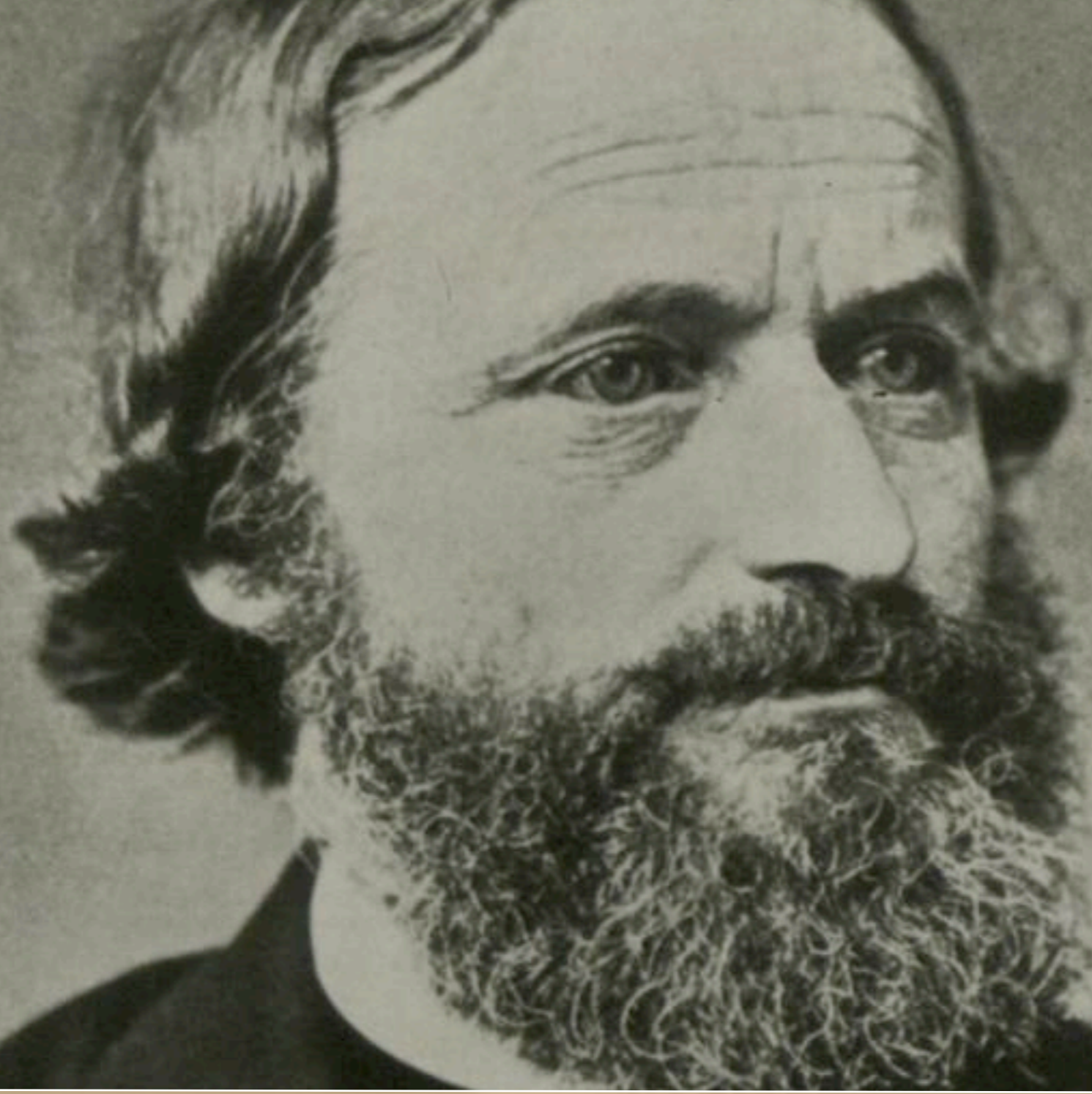


Analysis of Passive Circuits



Kirchoff's Voltage Law

The sum of the voltage changes in a loop must equal zero.



Kirchoff's Current Law


The sum of the currents flowing into and out of a node must equal zero.

series resistors




$$R = R_1 + R_2$$

parallel resistors

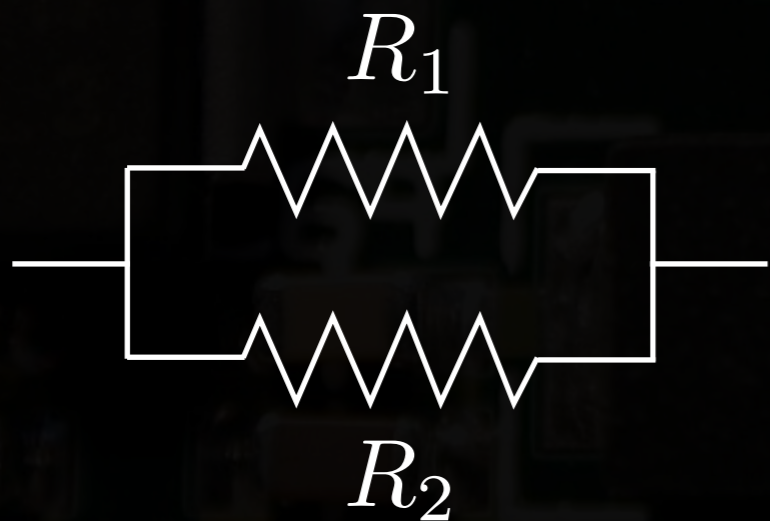


$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

series capacitors

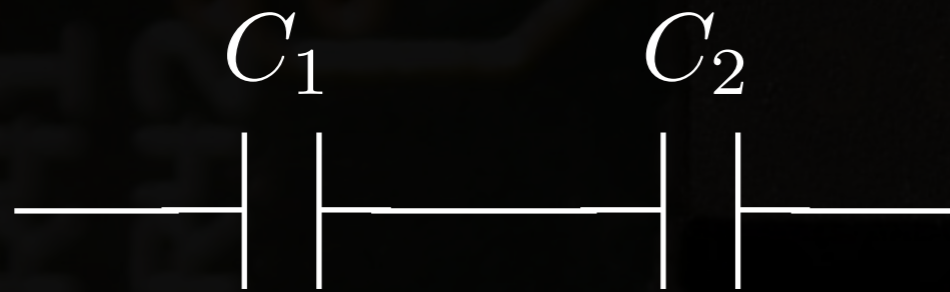

$$C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2}$$

parallel capacitors

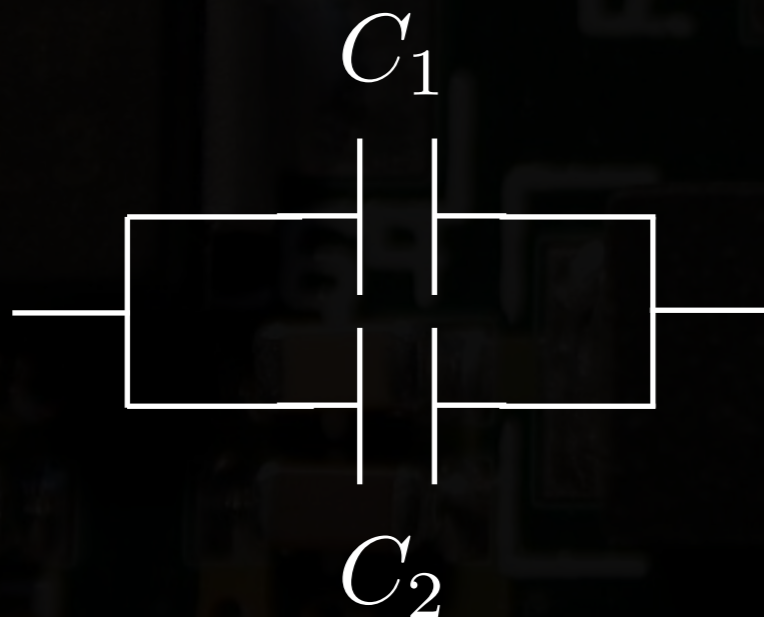


$$C = C_1 + C_2$$

series inductors



$$L = L_1 + L_2$$


parallel inductors

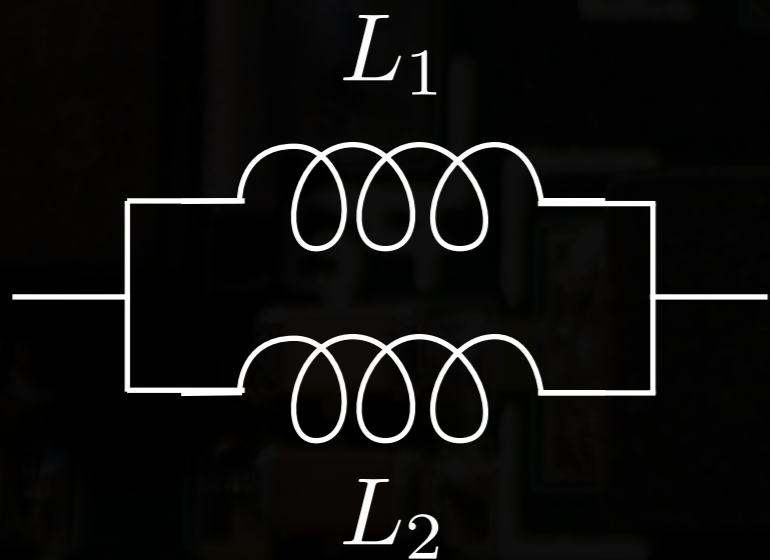

$$L = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} = \frac{L_1 L_2}{L_1 + L_2}$$

Voltage Divider

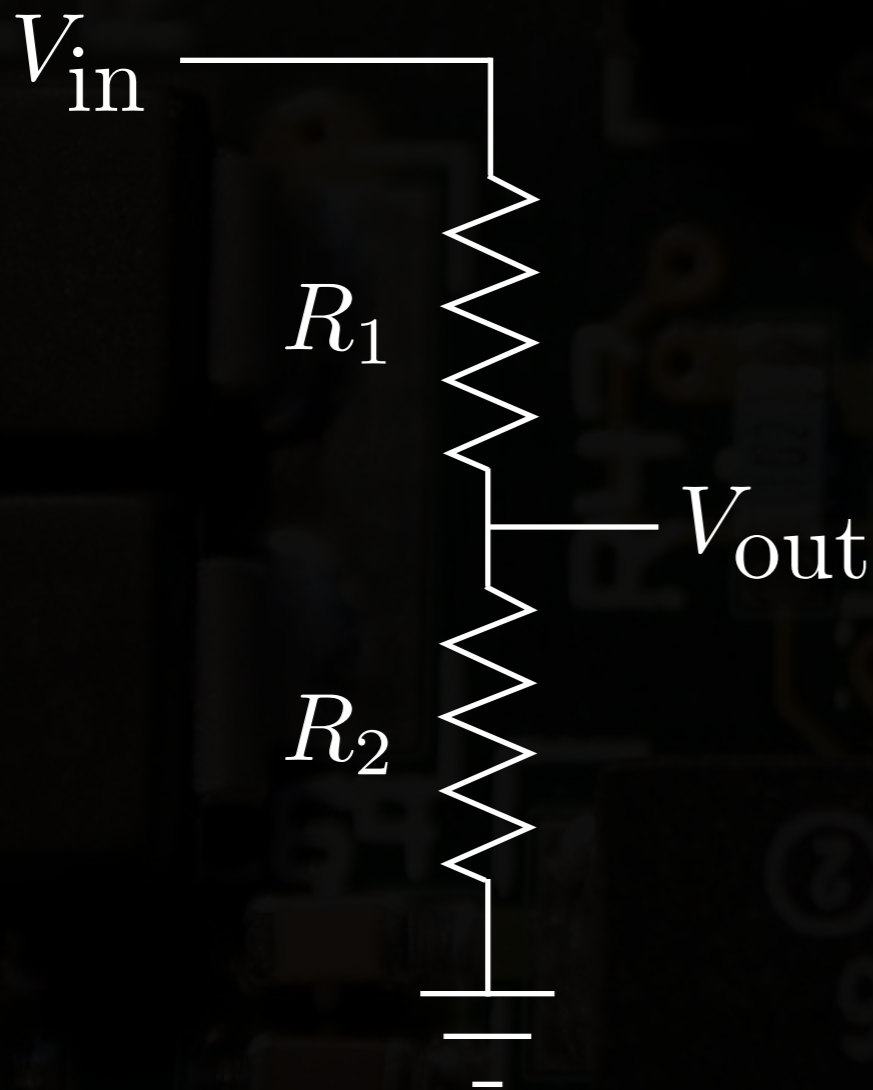Passive linear circuit that produces an output voltage that is a fraction of the input voltage.



$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

assuming the output
draws NO CURRENT

im•ped•ance |im'pēdns|

noun

the effective resistance of an electric circuit or component to alternating current, usually expressed as complex quantity $Z = R + jX$, where R is the resistance, and X is the reactance.

time-domain

impedance

resistor

$$V = IR$$

$$Z_R = R$$



inductor

$$V(t) = L \frac{dI}{dt}$$

$$Z_L = j\omega L$$



capacitor


$$V(t) = \frac{1}{C} \int_0^t I(\tau) d\tau$$

$$Z_C = \frac{1}{j\omega C}$$



Voltage Divider

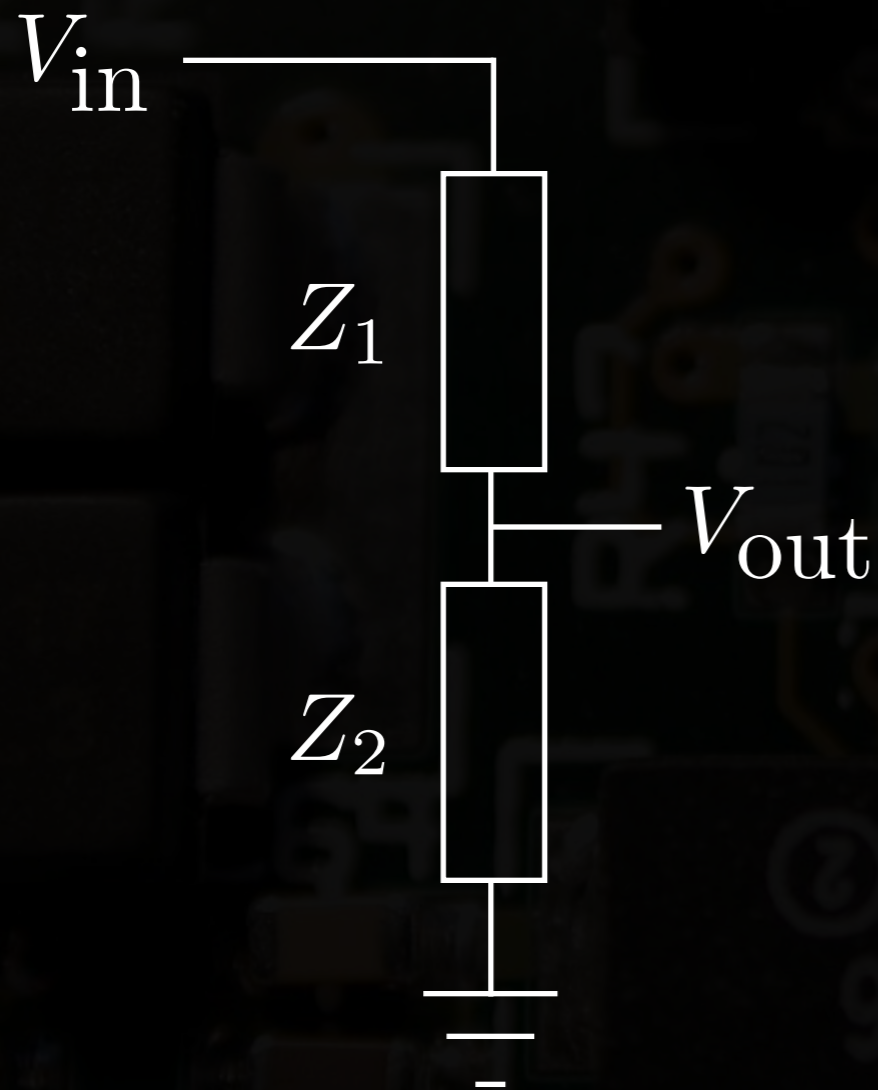Passive linear circuit that produces an output voltage that is a fraction of the input voltage.




$$V_{out} = \frac{Z_2}{Z_1 + Z_2} V_{in}$$

assuming the output
draws NO CURRENT

Voltage Divider

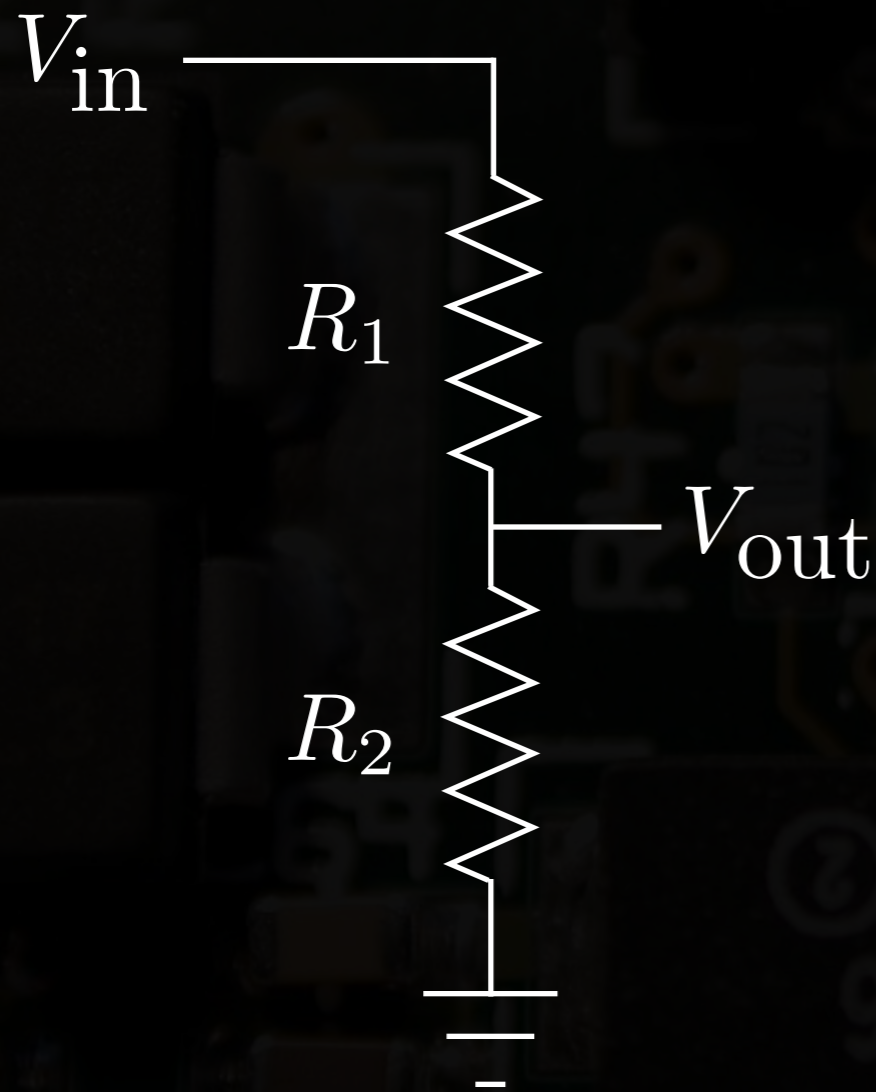A passive linear circuit that produces an output voltage that is a fraction of the input voltage.




$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

assuming the output
draws NO CURRENT

Low-Pass Filter

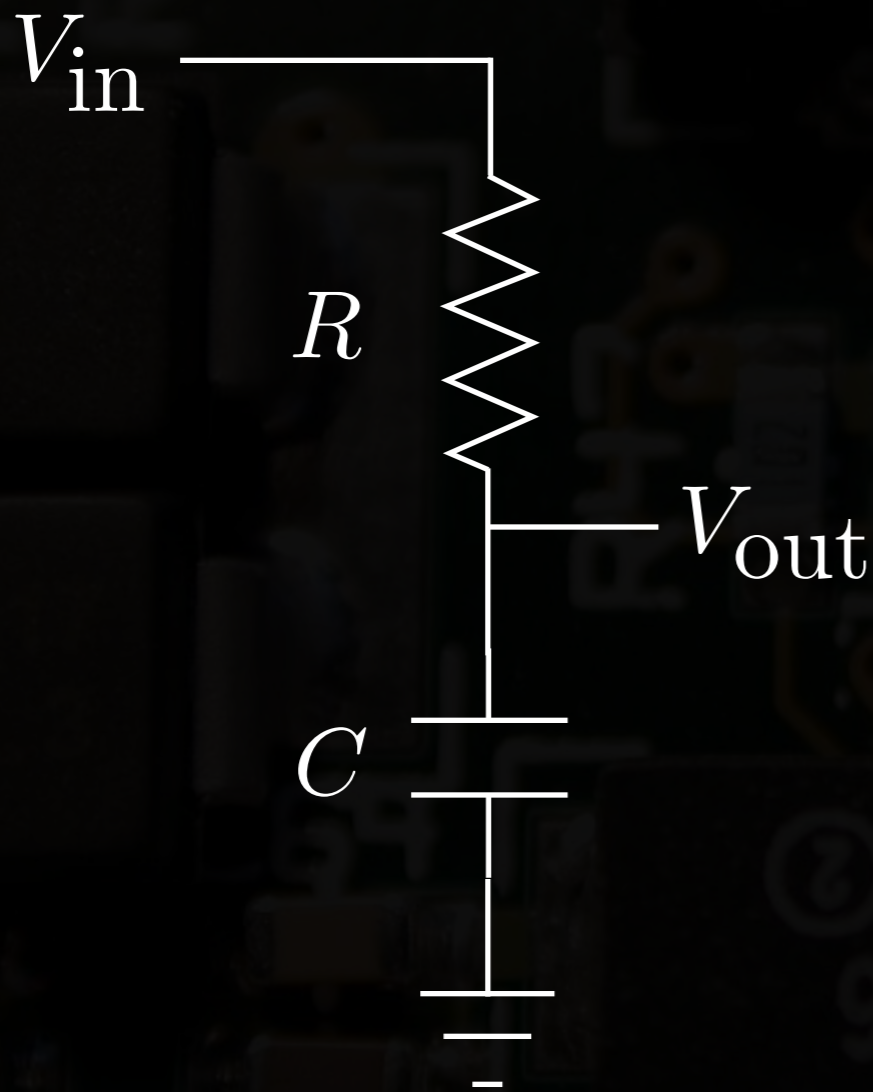A circuit in which lower-frequency signals are passed through, while higher-frequency signals are significantly attenuated.




$$V_{out} = \frac{1}{j\omega RC + 1} V_{in}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

assuming the output
draws NO CURRENT


Low-Pass Filter

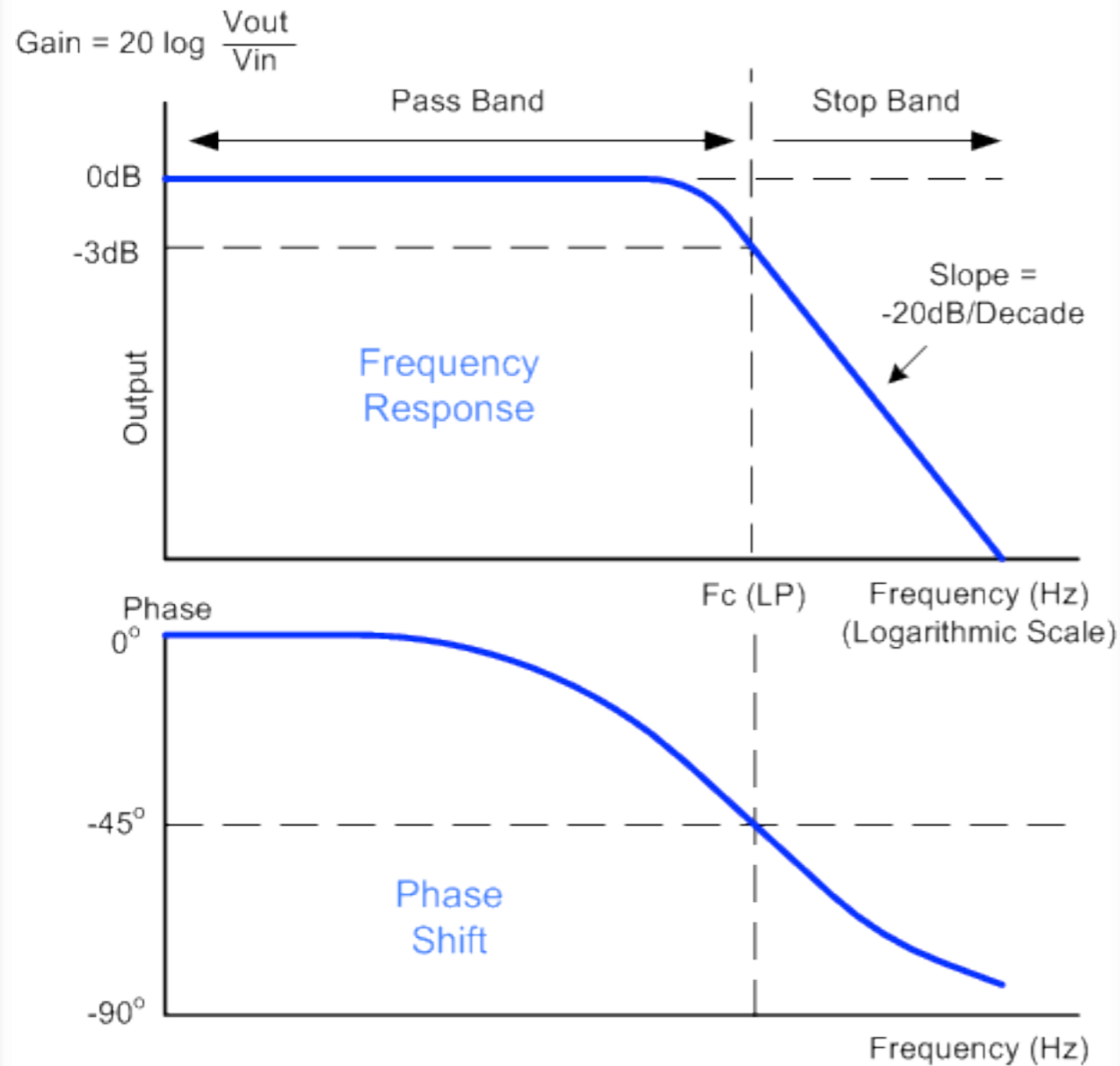A circuit in which lower-frequency signals are passed through, while higher-frequency signals are significantly attenuated.




-3dB cutoff frequency at:

$$f_c = \frac{1}{2\pi RC} \text{ (Hz)}$$

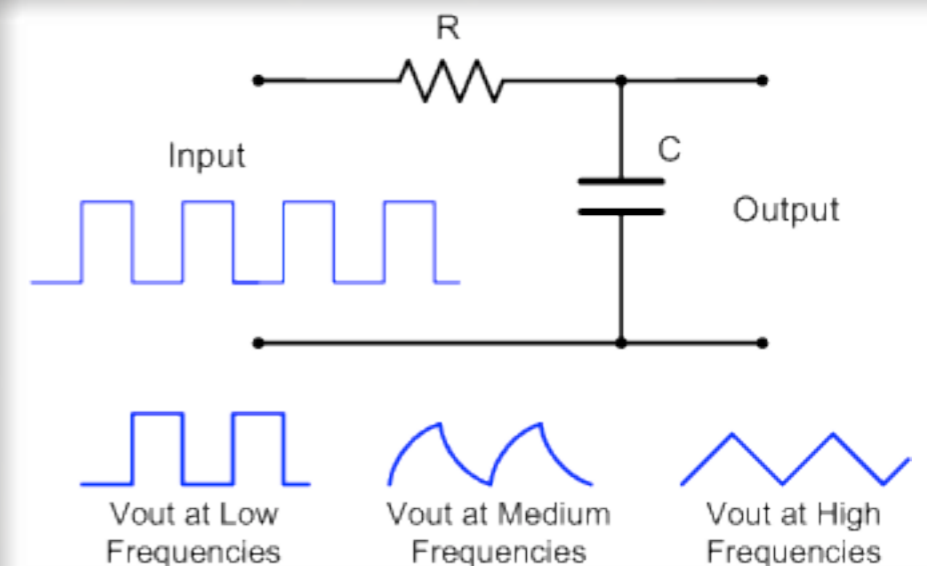

High-Pass Filter

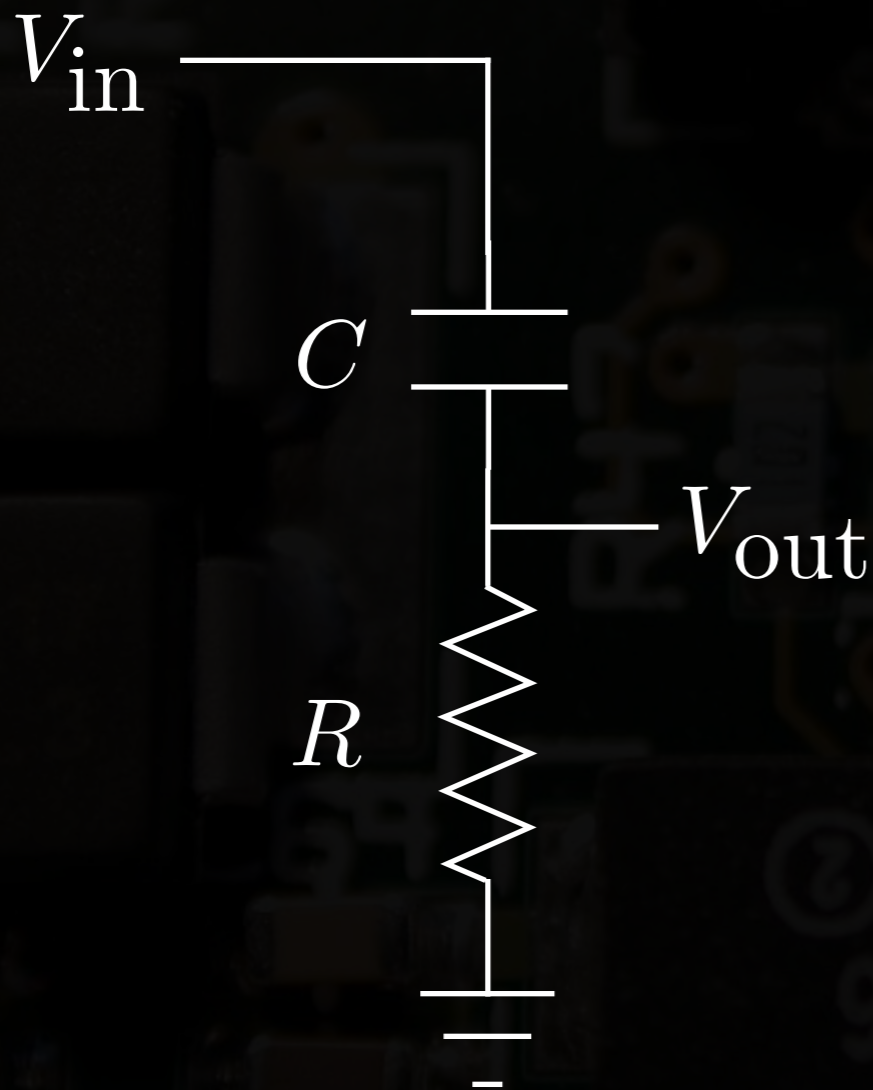a circuit in which higher-frequency signals are passed through, while lower-frequency signals are significantly attenuated.




$$V_{out} = \frac{j\omega RC}{j\omega RC + 1} V_{in}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

assuming the output
draws NO CURRENT

High-Pass Filter

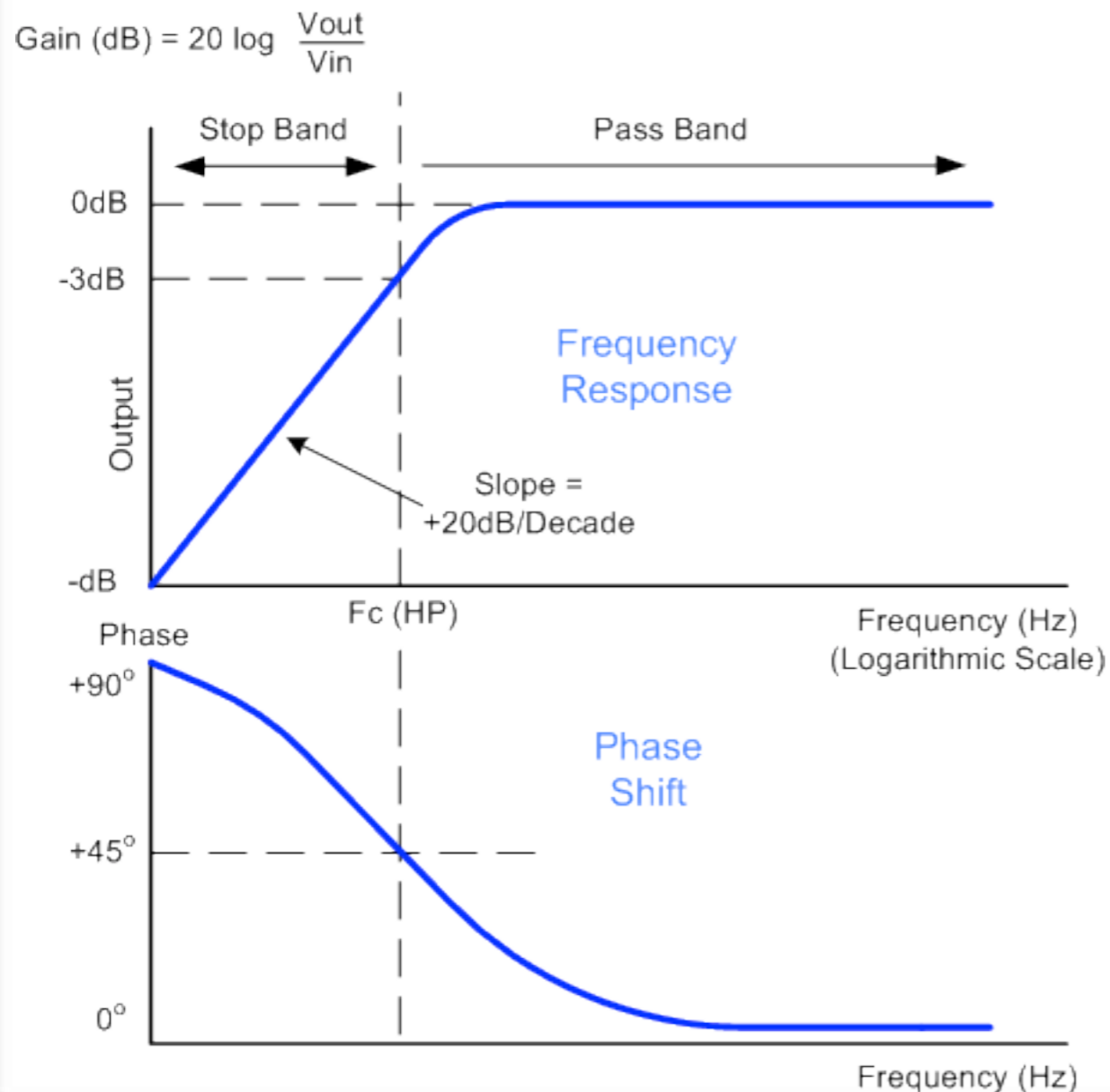a circuit in which higher-frequency signals are passed through, while lower-frequency signals are significantly attenuated.



-3dB cutoff frequency at:

$$f_c = \frac{1}{2\pi RC} \text{ (Hz)}$$

